

Jae Lee
ECEN 220
Lab #6 – Oscilloscope / Logic Analyzer
10/15/2013

Toggle Circuit Verilog Code

```
module Toggle(Qout, Clkout, Gclk, Clr);  
  
    input Gclk, Clr;  
    output Clkout, Qout;  
  
    wire temp1;  
  
    FF ff1(Qout, Gclk, Clr, temp1);  
  
    not(temp1, Qout);  
    buf(Clkout, Gclk);  
  
endmodule
```

Toggle Circuit Screen Capture




Time between two rises = 3ns

Toggle Circuit Question and answer

Analog signal doesn't have infinitely sharp slope. So If we zoom in enough, we should be able to see a steady rise of the signal.


Bounce Circuit Screen capture

 

Bounce Circuit Setting time

2.340ms


4-bit Shifter Screen capture

 

4-bit shifter pattern of values

7, 9, F, E, C, 3, 5, 0, 4, D, 1, 2, A, B, 6, 8 repeated.


16-bit Shifter Screen Capture(4290 Hex)

 

16-bit Shifter Pattern of Values(4290 Hex)

4290, 8521, 1A43, 34A6, 694C, D2B8, B570, 7AE0, F5E0, FBC1 and so on

 
16-bit Shifter Screen Capture(990ns after triggered pattern)



16-bit Shifter Value(990ns after triggered patter)

0B6B, 16F6, 2DED, 5BFA, B7D5, 7FAA and so on

 16-bit Shifter Screen Capture(16.38us after triggered pattern)



16-bit Shifter Value(16.38us after triggered pattern)

4290, 8521, 1A43, 34A6, 694C and so on

16-bit Shifter total number of values in repeating pattern

$16.38\mu s / .02\mu s = 819$

Anomalies

Oscilloscope sometimes combined signals together. I had to distribute manually. Also, I couldn't get 0x4290 starting point at first because scope 1 and 2 were set to not X.