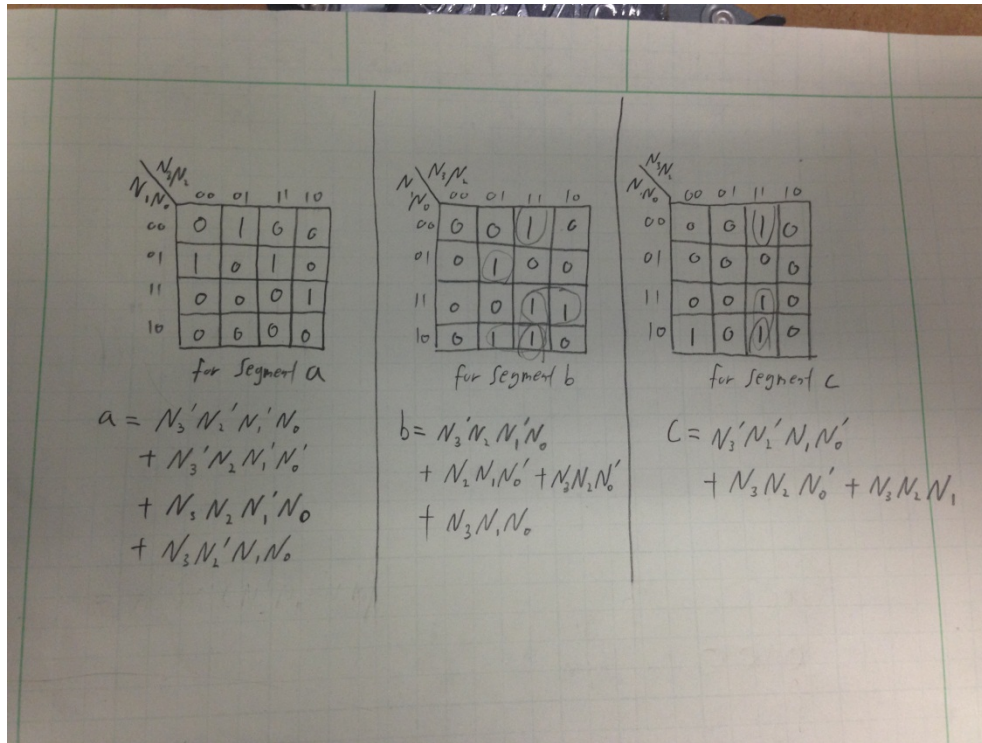


Jae Lee
ECEN 220
Lab #4
10/01/2013


Truth table for seven segment decoder

Input(High-asserted)				Output(Low-asserted)							LED
N3	N2	N1	N0	a	b	c	d	e	f	g	
0	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	1	0	0	1	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0	2
0	0	1	1	0	0	0	0	1	1	0	3
0	1	0	0	1	0	0	1	1	0	0	4
0	1	0	1	0	1	0	0	1	0	0	5
0	1	1	0	0	1	0	0	0	0	0	6
0	1	1	1	0	0	0	1	1	1	1	7
1	0	0	0	0	0	0	0	0	0	0	8
1	0	0	1	0	0	0	0	1	0	0	9
1	0	1	0	0	0	0	1	0	0	0	A
1	0	1	1	1	1	0	0	0	0	0	b
1	1	0	0	0	1	1	0	0	0	1	C
1	1	0	1	1	0	0	0	0	1	0	d
1	1	1	0	0	1	1	0	0	0	0	E
1	1	1	1	0	1	1	1	0	0	0	F


3 segment equations simplified using K-maps




ROM schematic

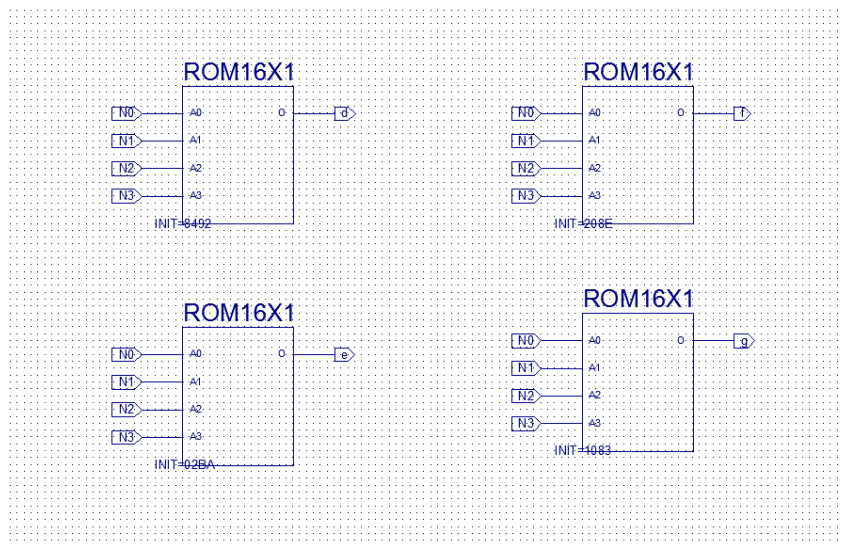

Combinational Logic Schematic

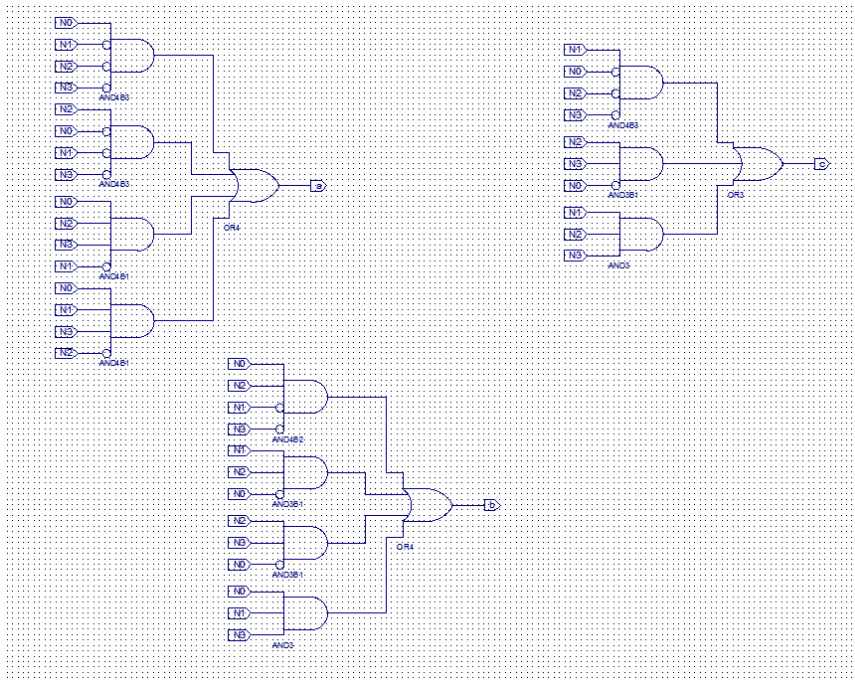

Seven Segment Decoder Schematic

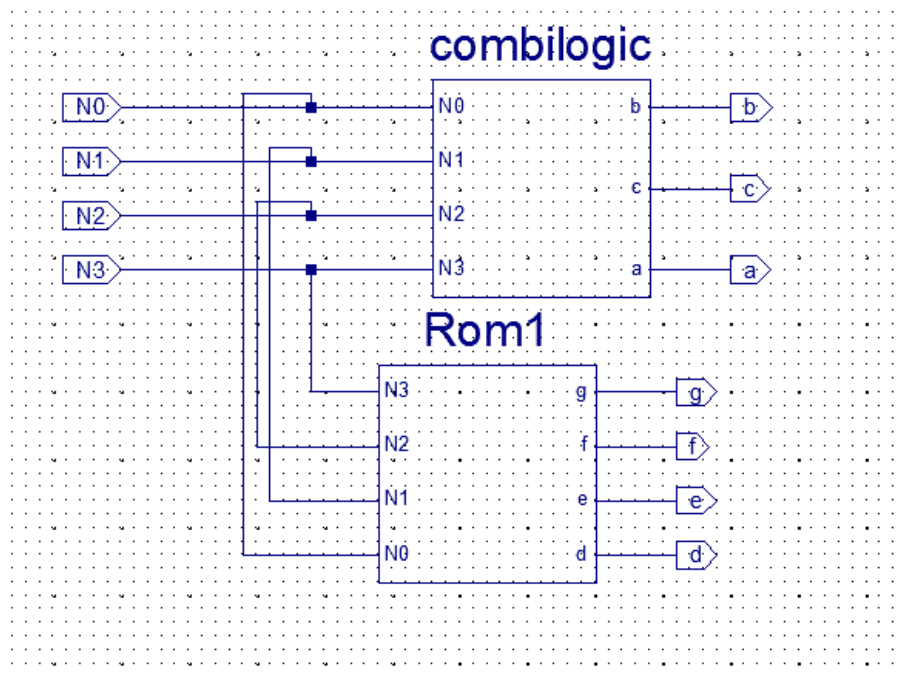

TCL files

wave add / -radix hex

isim force add N0 0 -time 0 -value 1 -time 10ns -repeat 20ns


isim force add N1 0 -time 0 -value 1 -time 20ns -repeat 40ns

isim force add N2 0 -time 0 -value 1 -time 40ns -repeat 80ns


isim force add N3 0 -time 0 -value 1 -time 80ns -repeat 160ns

run 160ns

Simulation waveforms

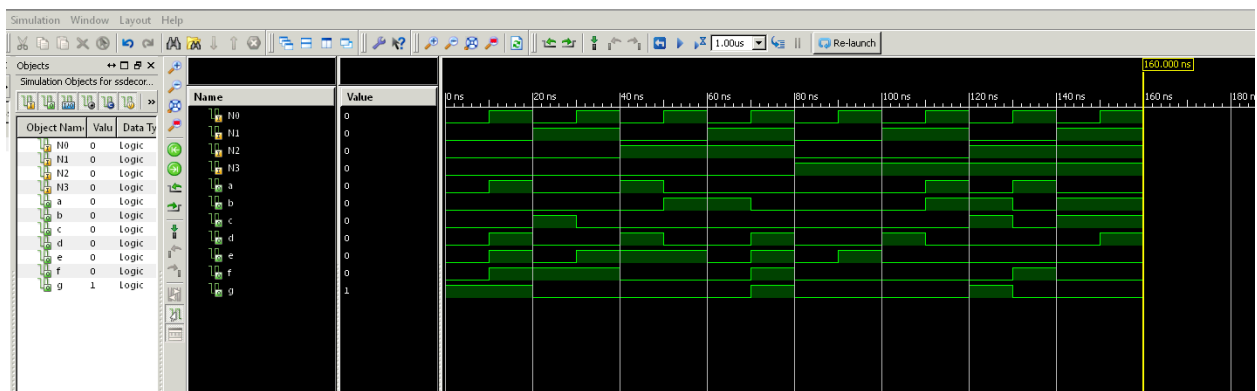

Test bench schematic

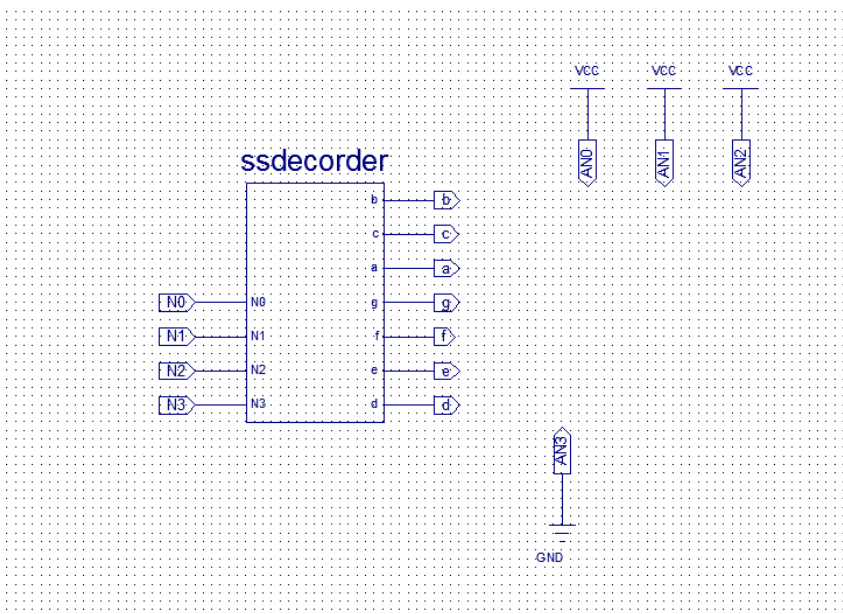

Test bench UCF file

Switches

#NET "sw<0>" LOC = "G18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW0

#NET "sw<1>" LOC = "H18"; # Bank = 1, Pin name = IP/VREF_1, Type = VREF, Sch name = SW1

#NET "sw<2>" LOC = "K18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW2

#NET "sw<3>" LOC = "L17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW3

NET N0 LOC = "L14"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW4

NET N1 LOC = "L13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW5

NET N2 LOC = "N17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW6

NET N3 LOC = "R17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW7

7 segment display

NET a LOC = "L18"; # Bank = 1, Pin name = IO_L10P_1, Type = I/O, Sch name = CA

NET b LOC = "F18"; # Bank = 1, Pin name = IO_L19P_1, Type = I/O, Sch name = CB

NET c LOC = "D17"; # Bank = 1, Pin name = IO_L23P_1/HDC, Type = DUAL, Sch name = CC

NET d LOC = "D16"; # Bank = 1, Pin name = IO_L23N_1/LDC0, Type = DUAL, Sch name = CD

NET e LOC = "G14"; # Bank = 1, Pin name = IO_L20P_1, Type = I/O, Sch name = CE

NET f LOC = "J17"; # Bank = 1, Pin name = IO_L13P_1/A6/RHCLK4/IRDY1, Type = RHCLK/DUAL, Sch name = CF

NET g LOC = "H14"; # Bank = 1, Pin name = IO_L17P_1, Type = I/O, Sch name = CG

#NET "dp" LOC = "C17"; # Bank = 1, Pin name = IO_L24N_1/LDC2, Type = DUAL, Sch name = DP

NET AN0 LOC = "F17"; # Bank = 1, Pin name = IO_L19N_1, Type = I/O, Sch name = AN0

NET AN1 LOC = "H17"; # Bank = 1, Pin name = IO_L16N_1/A0, Type = DUAL, Sch name = AN1

NET AN2 LOC = "C18"; # Bank = 1, Pin name = IO_L24P_1/LDC1, Type = DUAL, Sch name = AN2

NET AN3 LOC = "F15"; # Bank = 1, Pin name = IO_L21P_1, Type = I/O, Sch name = AN3

Anomalies

This lab was harder than all the labs so far. I encountered many errors when I was trying to overwrite symbols. Somehow Xilinx didn't overwrite. So I had to create a new source file and do the same thing. For TCL file, I accidentally included the capital W for waveform command which caused an error.