

Full Adder Verilog code

```
module FullAdder(  
    input A,  
    input B,  
    input Cin,  
    output Cout,  
    output Sum  
);  
  
    wire temp1,temp2,temp3;  
  
    xor(Sum,A,B,Cin);  
    and(temp1,A,B);  
    and(temp2,B,Cin);  
    and(temp3,A,Cin);  
    or(Cout,temp1,temp2,temp3);  
  
endmodule
```

4:1 Mux Verilog code

```
module Mux41(  
    output Q,  
    input A,  
    input B,  
    input C,  
    input D,  
    input Sel0,  
    input Sel1  
);  
  
    wire sel0bar,sel1bar,a1,b1,c1,d1;  
  
    not(sel0bar,Sel0);  
    not(sel1bar,Sel1);  
    and(a1,A,sel0bar,sel1bar);
```

```
and(b1,B,Sel0,sel1bar);
and(c1,C,sel0bar,Sel1);
and(d1,D,Sel0,Sel1);
or(Q,a1,b1,c1,d1);
```

endmodule

Full Adder TCL file

wave add / -radix hex

```
isim force add A 0 -time 0 -value 1 -time 10ns -repeat 20ns
isim force add B 0 -time 0 -value 1 -time 20ns -repeat 40ns
isim force add Cin 0 -time 0 -value 1 -time 40ns -repeat 80ns
```

run 80ns

4:1 MUX TCL file

wave add / -radix hex


```
isim force add A 0
isim force add B 1
isim force add C 0
isim force add D 1
isim force add Sel0 0 -time 0 -value 1 -time 20ns -repeat 40ns
isim force add Sel1 0 -time 0 -value 1 -time 40ns -repeat 80ns
```

run 80ns


```
isim force add A 1
isim force add B 0
isim force add C 1
isim force add D 0
```

run 80ns

Full Adder Simulation waveform

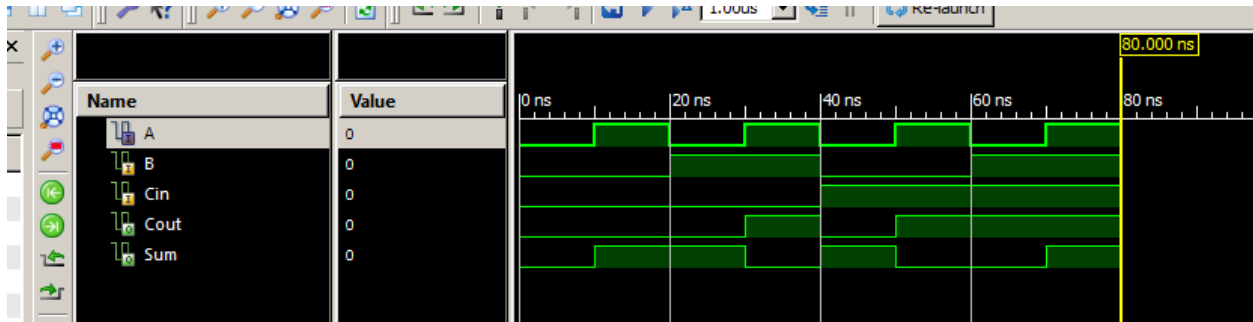

4:1 MUX Simulation waveform

 

1 bit ALU Verilog Code

```

module ALU(
    input C0,
    input C1,
    input Cin,
    input A,
    input B,
    output Cout,
    output Result
);

    wire tempCout,tempSum,c1,d1;

    FullAdder F1(A,B,Cin,tempCout,tempSum);
    Mux41 M1(Result,A,tempSum,c1,d1,C0,C1);
    CarryControl CC1(C0,C1,tempCout,Cout);
    and(c1,A,B);
    not(d1,A);

endmodule

module CarryControl(
    input C0,
    input C1,

```

```

input Cin,
output Cout
);
    wire temp1,temp2;

    not(temp1,C1);
    and(temp2,temp1,C0);
    and(Cout,temp2,Cin);

endmodule

```

1 bit ALU TCL file

wave add / -radix hex

```

isim force add A 0
isim force add B 0
isim force add Cin 0

```

```

isim force add C0 0 -time 0 -value 1 -time 20ns -repeat 40ns
isim force add C1 0 -time 0 -value 1 -time 40ns -repeat 80ns

```

run 80ns

```

isim force add A 1
isim force add B 0
isim force add Cin 0

```

run 80ns

```

isim force add A 0
isim force add B 1
isim force add Cin 0

```

run 80ns

```

isim force add A 1
isim force add B 1
isim force add Cin 0

```

run 80ns

```

isim force add A 1

```


```

isim force add B 1
isim force add Cin 1

```

run 80ns

1 bit ALU Simulation waveform

 

4 bit ALU Verilog code

```

module ALU4(
    input [1:0] C0,
        input Cin,
    input [3:0] A,
    input [3:0] B,
    output Cout,
    output [3:0] Result
);

    wire [2:0] tempCout;

    ALU a1(C0[0],C0[1],Cin,A[0],B[0],tempCout[0],Result[0]);
    ALU a2(C0[0],C0[1],tempCout[0],A[1],B[1],tempCout[1],Result[1]);
    ALU a3(C0[0],C0[1],tempCout[1],A[2],B[2],tempCout[2],Result[2]);
    ALU a4(C0[0],C0[1],tempCout[2],A[3],B[3],Cout,Result[3]);

endmodule

```

4 bit ALU TCL file

```
wave add / -radix hex
```

```

isim force add A 1010
isim force add B 0001
isim force add Cin 0

```

```

isim force add C0 00 -time 0ns -value 01 -time 20ns -value 10 -time 40ns -value 11 -time 60ns -repeat
80ns

```

run 80ns

isim force add A 1111

isim force add B 1010

isim force add Cin 0

run 80ns


isim force add A 0011

isim force add B 1100

isim force add Cin 0

run 80ns

4 bit ALU Simulation waveform

 

4 bit ALU UCF file

Leds

NET Result<0> LOC = "J14"; # Bank = 1, Pin name = IO_L14N_1/A3/RHCLK7, Type = RHCLK/DUAL, Sch name = JD10/LD0

NET Result<1> LOC = "J15"; # Bank = 1, Pin name = IO_L14P_1/A4/RHCLK6, Type = RHCLK/DUAL, Sch name = JD9/LD1

NET Result<2> LOC = "K15"; # Bank = 1, Pin name = IO_L12P_1/A8/RHCLK2, Type = RHCLK/DUAL, Sch name = JD8/LD2

NET Result<3> LOC = "K14"; # Bank = 1, Pin name = IO_L12N_1/A7/RHCLK3/TRDY1, Type = RHCLK/DUAL, Sch name = JD7/LD3

#NET "Led<4>" LOC = "E17"; # Bank = 1, Pin name = IO, Type = I/O, Sch name = LD4

#NET "Led<5>" LOC = "P15"; # Bank = 1, Pin name = IO, Type = I/O, Sch name = LD5

#NET "Led<6>" LOC = "F4"; # Bank = 3, Pin name = IO, Type = I/O, Sch name = LD6

NET Cout LOC = "R4"; # Bank = 3, Pin name = IO/VREF_3, Type = VREF, Sch name = LD7

Switches

NET B<0> LOC = "G18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW0

NET B<1> LOC = "H18"; # Bank = 1, Pin name = IP/VREF_1, Type = VREF, Sch name = SW1

NET B<2> LOC = "K18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW2

NET B<3> LOC = "K17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW3

```
NET A<0> LOC = "L14"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW4
NET A<1> LOC = "L13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW5
NET A<2> LOC = "N17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW6
NET A<3> LOC = "R17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW7
## Buttons
#NET "btn<0>" LOC = "B18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN0
#NET "btn<1>" LOC = "D18"; # Bank = 1, Pin name = IP/VREF_1, Type = VREF, Sch name = BTN1
NET C0<0> LOC = "E18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN2
NET C0<1> LOC = "H13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN3
```

Anomalies

It wasn't extremely difficult. I just had a trouble with setting a variable in array-form. It took a long time to finish, but I enjoyed.