

ECEN 220

Jae Lee

Lab 11 – LC3 Datapath

12/03/2013

### Datapath Verilog file (10pt)

```
module Datapath(  
    input reset,  
    input clk,  
    output [15:0] IR,  
    output N,  
    output Z,  
    output P,  
    input [1:0] aluControl,  
    input [2:0] SR1,  
    input [2:0] SR2,  
    input [2:0] DR,  
    input [1:0] selPC,  
    input [1:0] selEAB2,  
    input enaALU,  
    input regWE,  
    input enaMARM,  
    input selMAR,  
    input selEAB1,  
    input enaPC,  
    input ldPC,  
    input ldIR,  
    input ldMAR,  
    input ldMDR,  
    input selMDR,  
    input memWE,  
    input enaMDR,  
    input flagWE  
);  
    wire[15:0] Ra, Rb, aluOut, eabOut, PC, Buss, MARMuxOut, mdrOut;  
  
    ts_driver ts_dr0( MARMuxOut, Buss, enaMARM );  
    ts_driver ts_dr1( PC, Buss, enaPC );  
    ts_driver ts_dr2( mdrOut, Buss, enaMDR );  
    ts_driver ts_dr3( aluOut, Buss, enaALU );  
  
    ALU alu0(Ra, Rb, IR[5:0], aluControl, aluOut);  
    EAB eab(eabOut, IR[10:0], Ra, PC, selEAB1, selEAB2);  
    IR ir(IR, clk, ldIR, reset, Buss);  
    MARMux marmux(MARMuxOut, IR[7:0], eabOut, selMAR);  
    Memory mem0(mdrOut, Buss, clk, reset, ldMAR, ldMDR, selMDR, memWE);
```

```
NZP znp(N, Z, P, clk, flagWE, reset, Buss);  
PC pc(Buss, clk, reset, ldPC, eabOut, selPC, PC);  
RegFile reg0(Ra, Rb, Buss, clk, regWE, reset, DR, SR1, SR2);  
  
endmodule
```

### Master TCL file (2pt)

```
source wave.tcl  
  
isim force add clk 0 -time 0 -value 1 -time 5ns -repeat 10ns  
isim force add reset 1 -time 0 -value 0 -time 8ns  
run 12ns  
  
source fetch.tcl  
source and.tcl  
  
source fetch.tcl  
source add.tcl  
  
source fetch.tcl  
source not.tcl  
  
source fetch.tcl  
source br.tcl  
  
source fetch.tcl  
source jsr.tcl  
  
source fetch.tcl  
source ld.tcl  
  
source fetch.tcl  
source ld1.tcl  
  
source fetch.tcl  
source add1.tcl  
  
source fetch.tcl  
source st.tcl  
  
source fetch.tcl  
source jmp.tcl  
  
source fetch.tcl  
source br1.tcl  
  
source fetch.tcl
```

### Wave TCL file (2pt)

```

wave add clk
wave add reset
wave add Buss -radix hex

#add signals to view the PC and PC control
wave add selPC
wave add enaPC
wave add ldPC
wave add PC -radix hex

#add signals to view the IR and IR control
wave add ldIR
wave add IR -radix hex

#add signals to view the EAB control
wave add selEAB1
wave add selEAB2
wave add eabOut -radix hex

#add signals to view the MARMux control
wave add selMAR
wave add enaMARM
wave add MARMuxOut -radix hex

#add signals to view Register File control
wave add DR
wave add SR1
wave add SR2
wave add regWE

#add signals to view the Registers in the Register File
wave add /reg0/r0 -radix hex
wave add /reg0/r1 -radix hex
wave add /reg0/r2 -radix hex
wave add /reg0/r3 -radix hex
wave add /reg0/r4 -radix hex
wave add /reg0/r5 -radix hex
wave add /reg0/r6 -radix hex
wave add /reg0/r7 -radix hex
wave add Ra -radix hex
wave add Rb -radix hex

#add signals to view the ALU control
```

```
wave add aluControl
wave add enaALU
wave add aluOut -radix hex
```

```
#view the condition flags
wave add N
wave add Z
wave add P
wave add flagWE
```

```
#add signals to view the Memory Registers and the Memory control
wave add ldMAR
wave add /mem0/MARReg -radix hex
wave add ldMDR
wave add enaMDR
wave add selMDR
wave add mdrOut -radix hex
wave add /mem0/memOut -radix hex
wave add memWE
```

#### **Inactive TCL file (2pt)**

```
isim force add enaALU 0
isim force add enaMARM 0
isim force add enaPC 0
isim force add enaMDR 0
isim force add ldIR 0
isim force add ldPC 0
isim force add ldMAR 0
isim force add ldMDR 0
isim force add regWE 0
isim force add memWE 0
isim force add flagWE 0
```

#### **Fetch TCL file (2pt)**

```
source inactive.tcl

#fetch0
isim force add enaPC 1
isim force add ldMAR 1
run 10ns
source inactive.tcl

#fetch1
isim force add ldPC 1
isim force add selPC 00
isim force add ldMDR 1
isim force add selMDR 1
```

```
run 10ns
source inactive.tcl
```

```
#fetch2
isim force add ldIR 1
isim force add enaMDR 1
run 10ns
source inactive.tcl
```

### **All instruction TCL files (12pt)**

```
#add0
isim force add aluControl 01
isim force add SR1 000
isim force add DR 001
isim force add enaALU 1
isim force add regWE 1
isim force add flagWE 1

run 10ns
```

---

```
#add1
isim force add aluControl 01
isim force add SR1 010
isim force add SR2 001
isim force add DR 110
isim force add enaALU 1
isim force add regWE 1
isim force add flagWE 1

run 10ns
```

---

```
#and0
isim force add aluControl 01
isim force add SR1 000
isim force add DR 000
isim force add enaALU 1
isim force add regWE 1
isim force add flagWE 1

run 10ns
```

---

```
#br0
isim force add selPC 01
```

```
isim force add selEAB1 0
isim force add selEAB2 10
isim force add ldPC 1
```

```
run 10ns
```

---

```
#br1
isim force add selPC 01
isim force add selEAB1 0
isim force add selEAB2 10
isim force add ldPC 1
```

```
run 10ns
```

---

```
#jmp
isim force add SR1 111
isim force add selPC 01
isim force add selEAB1 1
isim force add selEAB2 00
isim force add ldPC 1
```

```
run 10ns
```

---

```
#jsr0
isim force add DR 111
isim force add regWE 1
isim force add enaPC 1
```

```
run 10ns
```

```
#jsr
source inactive.tcl
isim force add selEAB1 0
isim force add selPC 01
isim force add selEAB2 11
isim force add ldPC 1
```

```
run 10ns
```

---

```
#ld0
isim force add selEAB1 0
isim force add selEAB2 10
isim force add enaMARM 1
isim force add ldMAR 1
```

```
isim force add selMAR 0
```

```
run 10ns
```

```
#ld1
```

```
source inactive.tcl
```

```
isim force add ldMDR 1
```

```
isim force add selMDR 1
```

```
run 10ns
```

```
#ld2
```

```
source inactive.tcl
```

```
isim force add DR 010
```

```
isim force add regWE 1
```

```
isim force add flagWE 1
```

```
isim force add enaMDR 1
```

```
run 10ns
```

---

```
#ld0
```

```
isim force add selEAB1 0
```

```
isim force add selEAB2 10
```

```
isim force add enaMARM 1
```

```
isim force add ldMAR 1
```

```
isim force add selMAR 0
```

```
run 10ns
```

```
#ld1
```

```
source inactive.tcl
```

```
isim force add ldMDR 1
```

```
isim force add selMDR 1
```

```
run 10ns
```

```
#ld2
```

```
source inactive.tcl
```

```
isim force add DR 001
```

```
isim force add regWE 1
```

```
isim force add flagWE 1
```

```
isim force add enaMDR 1
```

```
run 10ns
```

---

```
#not
isim force add aluControl 11
isim force add DR 011
isim force add SR1 010
isim force add enaALU 1
isim force add regWE 1
isim force add flagWE 1

run 10ns
```

---

```
#st0
isim force add selEAB1 0
isim force add selEAB2 10
isim force add enaMARM 1
isim force add ldMAR 1

run 10ns
```

```
#st1
source inactive.tcl
isim force add aluControl 00
isim force add SR1 110
isim force add enaALU 1
isim force add ldMDR 1


run 10ns
```


```
#st2
source inactive.tcl
isim force add memWE 1


run 10ns
```


**Full Simulation waveform (10pt)**




 

 

 

 

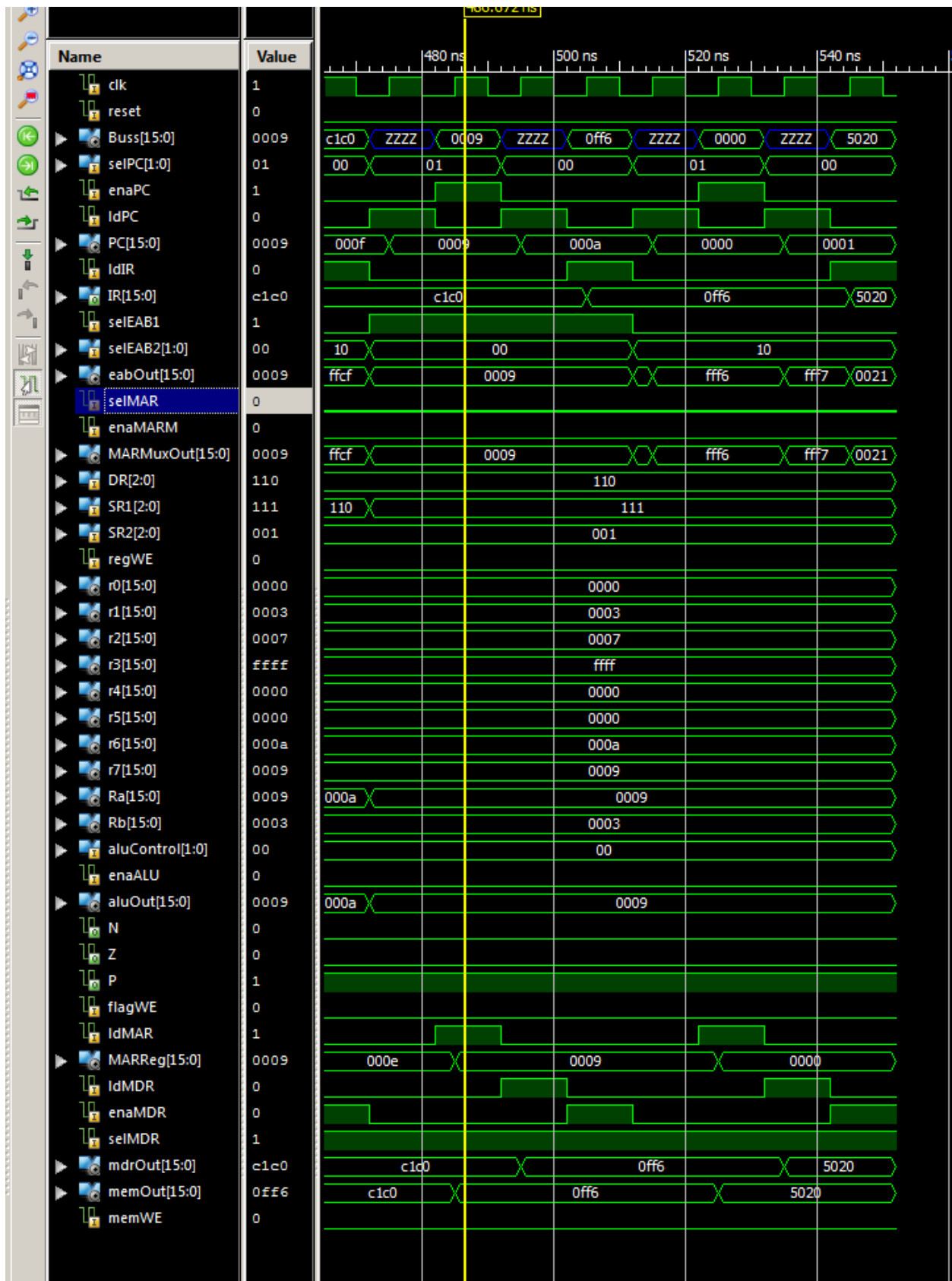

## **Anomalies**

This lab took so long. It took a while to figure out how to use ts\_driver in my datapath module. Also when I was making tcl files for the instructions, not resetting the enable signals gave us problems. Thank you TAs !!